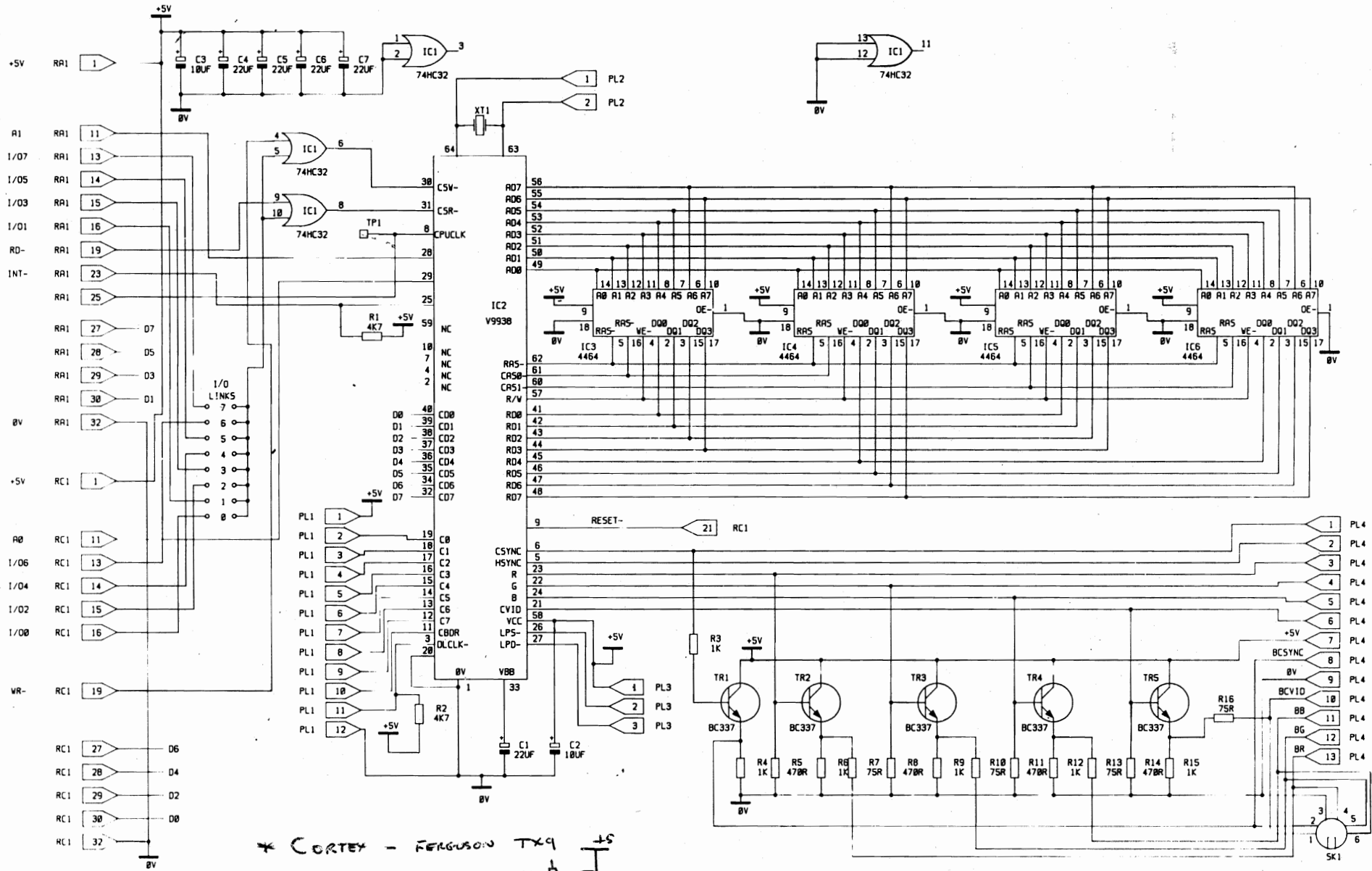


Figure 1. High Res circuit. September 1987 Maplin Magazine



* CORTEX - FERGUSON TX9

Handwritten circuit diagram showing a transistor (TR) with a resistor R3 in the base circuit and a resistor R4 in the emitter circuit. The output is labeled CSYNC.

Figure 1. High Res circuit.